

Operational Amplifiers (Op-Amps)


Author: John M. Cimbala, Penn State University
Latest revision: 22 October 2013

Introduction

- An **operational amplifier** (abbreviated **op-amp**) is an **integrated circuit (IC)** that amplifies the signal across its input terminals. Op-amps are *analog*, not *digital*, devices, but they are also used in digital instruments.
- Op-amps are widely used in the electronics industry, and are thus rather inexpensive – the ones used in the lab are about \$0.25 each!
- In this learning module, no details are given about the internal structure of the op-amp. Rather, we summarize many useful applications of op-amps.

Description of op-amps

- A triangle is used as the universal symbol for an op-amp (in schematic circuit diagrams), as shown to the right.
- The **supply voltage** terminals are at the top and bottom of the schematic diagram. Supply voltage is necessary because the op-amp requires power to run its internal circuitry. Both a positive and negative supply voltage are required, typically ± 15 V. In other words, $V_{\text{supply}}^+ = 15$ V, and $V_{\text{supply}}^- = -15$ V.
- In applications, any \pm voltage between about 10 to 20 V can be used for the supply voltage, depending on the manufacturer's specifications. (*Note:* We don't usually draw the supply voltages on circuit diagrams, but they must be connected or the op-amp will not work!)
- The **signal input** terminals are on the left – a **positive input** terminal V_p and a **negative input** terminal, V_n . However, the actual input voltages do *not* need to be positive and negative for inputs V_p and V_n , respectively.
- In fact, the V_p input is usually referred to as the **noninverting input** instead of the positive input, and the V_n input as the **inverting input** instead of the negative input, respectively.
- The connection for the **output voltage** V_o is on the right (pointed) side of the op-amp, as sketched above.

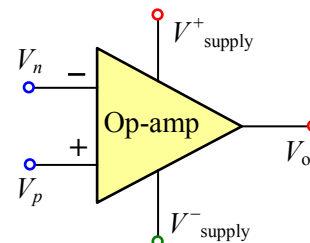

Ideal versus actual op-amps

- An **ideal op-amp** has **infinite input impedance**, and therefore it has **no effect on the input voltage**. This is called **no input loading**.
- An **actual** op-amp has **very high**, though not infinite, input impedance (typically millions of ohms), so that it has **little effect on the input voltage**. This is called **minimal input loading**.
- A direct result of the high input impedance is that we may assume **negligible current flowing into (or out of) either op-amp input, V_p or V_n** . This result helps us to analyze op-amp circuits, as discussed below.
- An ideal op-amp has **zero output impedance**, so that whatever is done to the output signal farther downstream in the circuit has **no affect on the output voltage** V_o . This is called **no output loading**.
- An actual op-amp has very low, though not zero, output impedance (typically a few Ω), so that what is done downstream of the op-amp has **little effect on the output voltage**. This is called **minimal output loading**.
- An ideal op-amp has infinite **gain, g** (Note that a lower case g is used here for the op-amp gain so as not to be confused with G , the gain of amplifier or filter *circuits*.) Op-amp gain g is called **open loop gain**.
- An actual op-amp has a very high, though not infinite, open loop gain; g is typically in the 10^5 to 10^6 range for the off-the-shelf op-amps that are commonly used in circuits.
- In the analysis of most of the circuits discussed below, the op-amps are approximated as ideal. The performance of an actual (real) op-amp is similar, but not exactly the same as that of an ideal op-amp.

Open-loop versus closed-loop configurations

- In an **open-loop configuration**, as in the above schematic diagram, $V_o = g(V_p - V_n)$.
- In other words, the output voltage V_o is a factor of g times the input voltage difference, $V_p - V_n$. This might be useful if the incoming signal is extremely small (microvolts), and in need of high amplification.
- In practice, however, circuits are most often built with a **feedback loop (closed-loop configuration)**, which forces the noninverting input and the inverting input to be nearly equal to each other, $V_p \approx V_n$.
- Without a feedback loop, the op-amp can easily **saturate** since g is large. **Saturation** means that **the output voltage clips at some maximum value**, typically a volt or so lower than supply voltage V_{supply}^+ .
- Likewise, saturation can occur at the low end as well, when **the output voltage clips at some minimum value**, typically a volt or so greater than supply voltage V_{supply}^- .

- **Example:**

Given: The gain of an op-amp is 1 million ($g = 1 \times 10^6$). The high supply voltage V_{supply}^+ is 15.0 V. The op-amp saturates at 13.9 V.

To do: Calculate the input voltage difference ($V_p - V_n$) that will cause saturation when the op-amp is operated in an open-loop configuration.

Solution: From the open-loop gain equation, $(V_p - V_n) = \frac{V_o}{g} = \frac{13.9 \text{ V}}{1 \times 10^6} = 1.39 \times 10^{-5} \text{ V} = 13.9 \mu\text{V}$.

Thus, **Any voltage difference greater than 13.9 μV will saturate the op-amp.**


Discussion: Note how easily an op-amp is saturated. This is why the open-loop configuration is rarely used.

Closed-loop op-amp circuits

- Almost all practical circuits utilize op-amps **in a closed-loop configuration to avoid op-amp saturation**.
- In all of the examples below, there is **feedback** from the output terminal of the op-amp to one of the input terminals. (This is what makes the configuration a *closed-loop* configuration.)
- In the analyses to follow, it is assumed that $V_n \approx V_p$ because of the feedback loop, and because we approximate the op-amps as nearly ideal. This will be better understood as these circuits are analyzed.
- **Note:** In all the schematic diagrams to follow, the supply voltages V_{supply}^+ and V_{supply}^- are *not* shown, but you must remember to wire these to the op-amp, or it will not work!


Buffer (also called a **voltage follower**)

- **Purpose:** To provide high impedance for a voltage signal.
- **Schematic:**
 - A **circuit diagram** or **schematic** of a buffer is shown to the right.
 - Note the symbol for **ground** at the bottom of the schematic diagram.
 - In a buffer, the output is fed directly back into the inverting input terminal to provide the feedback loop.
 - The voltage signal is fed directly into the noninverting input terminal.
- **Analysis:**
 - Since the op-amp output is connected directly to the inverting input, $V_{\text{out}} = V_o = V_n$.
 - If the op-amp were *ideal*, $V_n = V_p = V_{\text{in}}$, and, $V_{\text{out}} = V_{\text{in}}$. For a *real* op-amp, $V_n \approx V_p = V_{\text{in}}$, and $V_{\text{out}} \approx V_{\text{in}}$.
- **Discussion:**
 - What have we accomplished? At first it appears that *nothing has been accomplished at all*, since the output voltage is simply equal to the input voltage! Why do we even need a buffer in the first place?
 - Actually, a buffer is very important when the input signal needs to be **isolated** from the rest of the circuit.
 - Because of the high input impedance of the op-amp, the buffer causes V_{in} to be **insensitive to anything that happens downstream in the circuit**.
 - For example, suppose the signal must be connected to something that draws a *current*. Without the buffer, V_{in} would be affected by the current draw. With the op-amp buffer in place, however, the current draw has no effect on input signal V_{in} .
 - Because of the low output impedance of the op-amp, the output voltage V_{out} is likewise not affected significantly by the current draw; V_{out} **remains nearly equal to V_{in} regardless of the downstream circuit**.

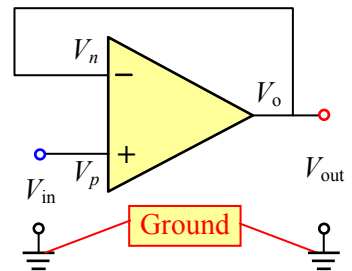

Inverting amplifier

- **Purpose:** To multiply (and invert) a voltage signal by some factor.
- **Schematic:**
 - A schematic of an inverting amplifier is shown to the right.
 - The input signal comes into the *negative* (inverting) input of the op-amp, after first passing through resistor R_1 .
 - Since current flows from the input (at voltage V_{in}) through resistor R_1 , and then to the op-amp input (at zero voltage), the input impedance of this op-amp circuit is about the same as R_1 .
 - The resistors are typically around 10 k Ω to 100 k Ω .
 - The output impedance of this op-amp circuit is on the order of one ohm.
- **Analysis:**
 - Since negligible current flows into the op-amp at input V_n , the *same* current (I) flowing through the first resistor also flows through the second resistor, as shown.

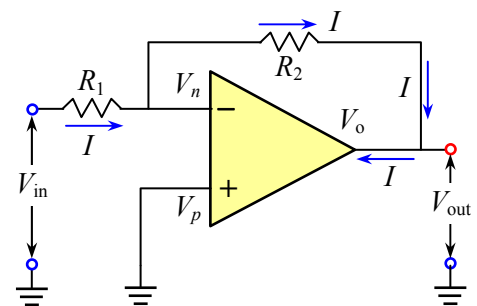

- Since we assume that V_{out} is measured by a *voltmeter, oscilloscope, or data acquisition system with very high input impedance*, all of this current (I) must flow *into* the output terminal of the op-amp, as shown.
- The sign of the current is assumed, as sketched in the diagram. If V_{in} is positive, this assumption is correct. If V_{in} is negative, the current is of opposite sign to that shown.
- Using Ohm's law, $V_{in} - IR_1 = V_n$.
- But, for ideal op-amp behavior, $V_n = V_p = 0$, since V_p is *grounded*. [For a real op-amp, $V_n \approx V_p = 0$.]
- Thus, solving for the current, $I = V_{in}/R_1$.
- In the feedback portion of the circuit, $V_o = V_n - IR_2 = 0 - IR_2 = -(V_{in}/R_1)R_2$.

- Or, finally, $V_{out} = V_o = -\frac{R_2}{R_1}V_{in} = GV_{in}$, where the **gain G** of any amplifier is defined as $G = \frac{V_{out}}{V_{in}}$.

- The gain of our *inverting* amplifier turns out to be the negative ratio of R_2 to R_1 , i.e., $G = \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$.

- **Discussion:**


- Resistors R_1 and R_2 can be chosen to achieve any desired gain. If R_2 is greater than R_1 , the signal is **amplified** (and inverted)
- The magnitude of the gain does not necessarily have to be greater than unity. An inverting amplifier can actually **attenuate** (and invert) a signal if R_2 is less than R_1 .

Inverter

- **Purpose:** **Invert (change the sign) of a signal without amplification or attenuation.**

- **Schematic:**

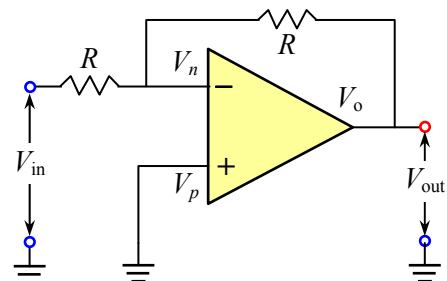- A schematic diagram of an inverter is shown to the right.
- The schematic diagram is identical to that above for the inverting amplifier. The only difference is that R_1 and R_2 have the same value, and are indicated simply as R .



- **Analysis:**

- The analysis is the same as above.
- For identical R_1 and R_2 , the gain is $G = -R_2/R_1 = -1$. Thus, $V_{out} = V_o = -V_{in}$.

- **Discussion:**


- An inverter simply changes the sign of a signal. It also acts as a *buffer*, so all of the advantages of the buffer listed above apply here as well. We could instead call the inverter an **inverting buffer**.

Inverting summer

- **Purpose:** **To add (and invert) two voltage signals.**

- **Schematic:**

- A schematic diagram is shown to the right.
- All three resistors in this circuit have the same value, typically around 10 k Ω to 100 k Ω .
- The actual value of R is not critical. However, in typical circuits, resistors lower than 1 k Ω are generally *not* used because they waste power unnecessarily.
- Likewise, resistors higher than 1 M Ω are generally *not* used because they can lead to stray capacitance effects, details of which are beyond the scope of the present discussion.

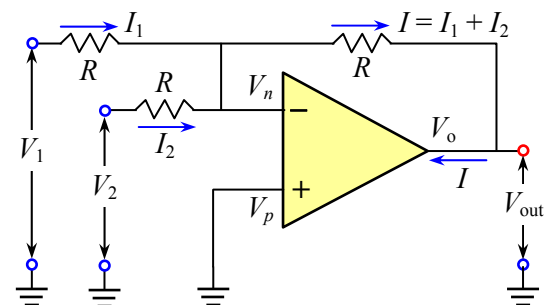

- **Analysis:**

- We examine the input (left) side of the op-amp first (using Ohm's law): $V_1 - I_1R = V_2 - I_2R = V_n$.
- But, if the op-amp is nearly ideal, $V_n \approx V_p = 0$ (since V_p is *grounded*). Thus, $V_1 = I_1R$ and $V_2 = I_2R$.
- Now we examine the output (right) side, again using Ohm's law, and utilizing the fact that negligible current flows into the op-amp at input V_n (hence, the current flowing through the top right resistor is approximately equal to $I_1 + I_2$). Therefore, $V_o = V_n - (I_1 + I_2)R = 0 - I_1R - I_2R = -V_1 - V_2$.
- Or, finally, $V_{out} = V_o = -(V_1 + V_2)$.

- **Discussion:**

- The two input voltages V_1 and V_2 have been added, but the output is the *negative* of the sum – hence the name *inverting summer*.

- This is a very effective and *safe* way to perform a summation of two voltages. The main advantage is due again to the high input impedance of the op-amp – voltages V_1 and V_2 are *isolated* in this summing circuit. That is, they are not affected by what happens *downstream* of the op-amp or by *each other*.
- The inversion (negative sign) of the signal is not a problem. If the negative sign needs to be removed, it can be done so with a simple inverter, as discussed above.

- **Example:**

Given: Some op-amps and a bunch of 20-kohm resistors are available in the lab.


To do: Show how these components can be used to *double the voltage of an input signal*. Use *inverting* circuits, and draw the circuit diagram.

Solution:

- We use an inverting amplifier to produce the gain. Then we use an inverter in series to remove the negative sign produced by the inverting amplifier.

- If R_1 is selected as 20 k Ω , R_2 must be 40 k Ω to achieve amplification by a factor of two. Two resistors in series will do the job nicely.

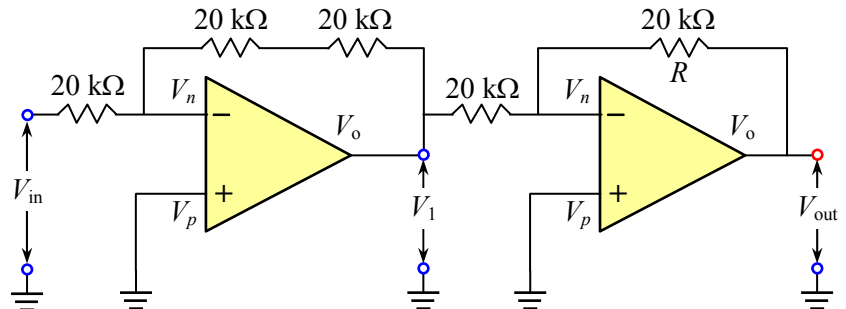- The available resistors can also be used for the inverter.
- The schematic diagram is shown to the right.



- The left half of the circuit is the **inverting amplifier**, with a gain of $G = -\frac{R_2}{R_1} = -\frac{40 \text{ k}\Omega}{20 \text{ k}\Omega} = -2$.

- The output voltage from the first op-amp is labeled V_1 , and $V_1 = GV_{in} = -2V_{in}$.

- The right half of the circuit is the **inverter**, with $V_{out} = -V_1$. Thus $V_{out} = 2V_{in}$ as desired.

Discussion: The above circuit requires 2 op-amps and 5 resistors. If we use a noninverting amplifier instead, as discussed next, we can achieve the same result with just 1 op-amp and 2 resistors.

Noninverting amplifier

- **Purpose:** To amplify a voltage signal *without inverting*.

- **Schematic:**

- A schematic of a noninverting amplifier is shown to the right.
- As seen, the noninverting amplifier is similar to the inverting amplifier except that the input signal comes into the *positive* (noninverting) input of the op-amp instead of into the negative (inverting) input.

- The input impedance of this op-amp circuit is on the order of hundreds of megaohms (the input impedance of a noninverting amplifier is equal to the internal impedance of the op-amp itself).

- The output impedance of this op-amp circuit is on the order of one ohm.

- **Analysis:**

- Since negligible current flows into the op-amp at input V_n , the *same* current (I) flowing through the first resistor also flows through the second resistor, as shown.

- Assuming that V_{out} is measured by a *voltmeter*, *oscilloscope*, *data acquisition system*, etc. with *very high input impedance*, all the current (I) must flow *out* of the output terminal of the op-amp, as shown.

- The sign of the current is assumed, as sketched in the diagram. If V_{in} is positive, this assumption is correct. If V_{in} is negative, the current is of opposite sign to that shown.


- For ideal op-amp behavior, $V_n = V_p = V_{in}$ (since V_{in} is wired to V_p). [For a real op-amp, $V_n \approx V_p = V_{in}$.]

- Using Ohm's law, $V_n - IR_1 = V_{in} - IR_1 = 0$ since the left-most wire of the circuit is *grounded*.

- Thus, solving for the current, $I = V_{in}/R_1$.

- In the feedback portion of the circuit, $V_o = V_n + IR_2 = V_{in} + IR_2 = V_{in} + (V_{in}/R_1)R_2$.

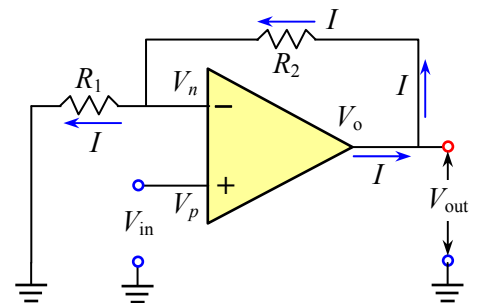- Finally, $V_{out} = V_o = \left(1 + \frac{R_2}{R_1}\right)V_{in} = GV_{in}$, where the **gain** of a *noninverting* amplifier is $G = \frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$.



- **Example:**

Given: Some op-amps and a bunch of 20-kohm resistors are available in the lab.


To do: Show how these components can be used to *double the voltage of an input signal*. Use *noninverting* circuits, and draw the circuit diagram.

Solution:

- We use a noninverting amplifier to produce the gain.
- If R_1 is selected as 20 k Ω , R_2 must also be 20 k Ω to achieve amplification by a factor of two.
- The schematic diagram is shown to the right.
- The gain of this **noninverting amplifier** is

$$G = 1 + \frac{R_2}{R_1} = 1 + \frac{20 \text{ k}\Omega}{20 \text{ k}\Omega} = 2.$$

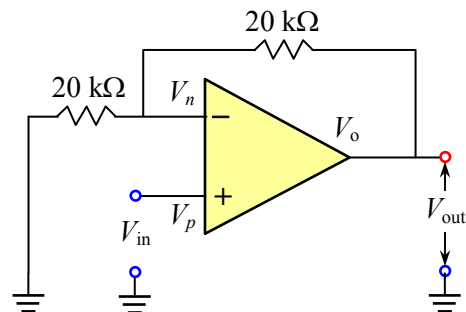- Thus, $V_{\text{out}} = GV_{\text{in}}$, or $V_{\text{out}} = 2V_{\text{in}}$ as desired.




Discussion: The above circuit requires only 1 op-amp and 2 resistors. Compare this to the previous example using inverting circuits, where we needed 2 op-amps and 5 resistors to achieve the same result.

First-order, active, low-pass, inverting filter

- **Purpose:** To low-pass filter (and invert) a voltage signal.

- **Schematic:**

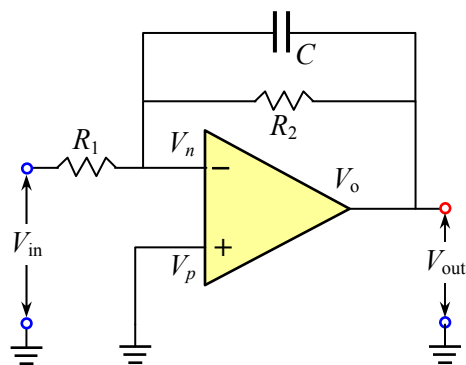- The schematic is shown to the right.
- As seen, a first-order, active, low-pass, inverting filter is simply an inverting amplifier with a capacitor added in parallel to the resistor in the feedback loop.
- You are invited to compare this filter circuit with that of a simple passive first-order RC low-pass filter circuit.



- **Analysis:**

- We consider the simplest case in which the resistor values are chosen to be identical ($R_1 = R_2 = R$); there is *no amplification*.
- At *low frequencies*, the capacitor acts like an *open switch*, and thus does not contribute anything. The circuit is then *the same as an inverter*, with $V_{\text{out}} \approx -V_{\text{in}}$, and **low frequencies pass unaffected** (except that the signal is *inverted*).
- At *high frequencies*, the capacitor acts like a *closed switch*, rendering R_2 useless, and forcing V_o to nearly equal V_n . However, V_p is grounded, so $V_{\text{out}} = V_o \approx V_n \approx V_p = 0$. In other words, **high frequencies are attenuated significantly** – the output voltage is nearly zero.
- It turns out that at *intermediate frequencies*, this circuit behaves as a **first-order Butterworth low-pass filter**. The equation for the gain G of the filter is the same as that defined previously for a simple RC filter, except for the negative sign. The phase shift is also the same as that defined previously.
- The **cutoff frequency** of this active filter is in fact the same as that for a simple, passive, first-order, low-pass RC filter,

$$f_{\text{cutoff}} = \frac{\omega_{\text{cutoff}}}{2\pi} = \frac{1}{2\pi R_2 C}.$$

Notice that R_2 is used here rather than R_1 .

- **Discussion:**


- If a simple RC circuit is used for filtering, the filter is called a **passive filter**.
- When an op-amp with feedback is used, as in the present case, the filter is called an **active filter**.
- As with an inverting amplifier, values of R_2 and R_1 can be selected such that there is *amplification* (or *attenuation*) of the signal as well.
- If the negative sign is a problem, we can add a simple inverter in series. Or, we can use noninverting circuitry instead.

First-order, active, high-pass, inverting filter

- **Purpose:** To high-pass filter (and invert) a voltage signal.

- **Schematic:**

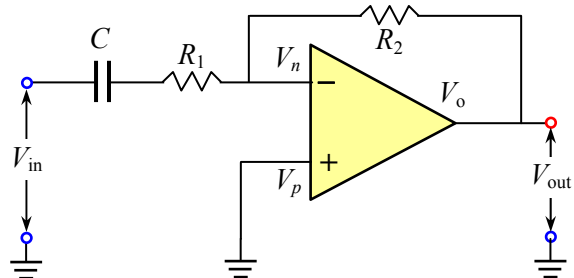- The schematic is shown to the right.
- The first-order, active, high-pass, inverting filter is similar to the first-order, active, low-pass, inverting filter discussed above, except that the capacitor is



placed in *series* with the *input* resistor instead of in *parallel* with the *feedback* resistor.

- **Analysis:**

- If the resistor values are chosen to be identical ($R_1 = R_2 = R$), there is *no amplification*.
- At *low frequencies*, the capacitor acts like an *open switch*, so V_{in} is effectively isolated from the output.
- Another way to look at this case is that at low frequencies, no current can flow through the capacitor or through resistor R_1 . Thus, $V_{out} = V_n \approx V_p = 0$ since V_p is grounded; **low frequencies are attenuated**.
- At *high frequencies*, the capacitor acts like a *closed switch*, having no effect on the circuit. The circuit then becomes the same as an inverter, with $V_{out} = -V_{in}$; **high frequencies pass unaffected** (except that the signal is *inverted*).
- It turns out that at *intermediate frequencies*, this circuit behaves as a **first-order Butterworth high-pass filter**. The equation for the gain G of the filter is the same as that defined previously for a simple RC filter, except for the negative sign. The phase shift is also the same as that defined previously.
- The **cutoff frequency** of this active filter is in fact the same as that for a simple, passive, first-order, low-pass RC filter, $f_{cutoff} = \frac{\omega_{cutoff}}{2\pi} = \frac{1}{2\pi R_1 C}$. Notice that R_1 is used here rather than R_2 .

- **Discussion:**


- Since an op-amp with a feedback loop is used in the present case, the filter is an **active filter**.
- As with an inverting amplifier, values of R_2 and R_1 can be selected such that there is *amplification* (or *attenuation*) of the signal as well.
- If the negative sign is a problem, we can add a simple inverter in series. Or, we can use noninverting circuitry instead.

Low-voltage clipping circuit

- **Purpose:** To clip voltages below some reference voltage, V_{ref} .

- **Schematic:**


- The schematic is shown to the right.
- The noninverting input of the op-amp is connected to the **reference voltage** V_{ref} .
- The component just to the right of the op-amp is called a **switching diode**.
- A switching diode allows current to flow **in one direction only** (in the direction of the small triangle – to the right in the orientation shown here), and **blocks currents from flowing the opposite way**.

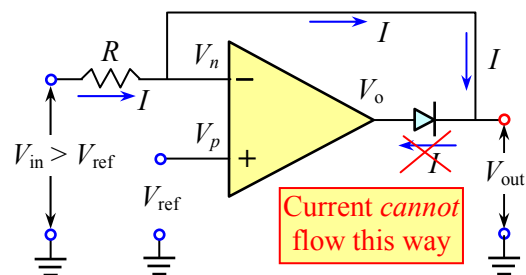

- **Analysis:**


- **If $V_{in} > V_{ref}$**
 - Current tries to flow through resistor R in the direction indicated on the above diagram.
 - No current can flow into the left side (input side) of the op-amp, because of its high input impedance.
 - Likewise, no current can flow downstream from (to the right of) V_{out} because it is assumed that V_{out} either goes into another high-impedance component, such as another op-amp, or is being measured with a high impedance voltmeter, oscilloscope, digital data acquisition system, etc.
 - Thus, the only path for the current to flow is *through the feedback loop* and back into the output (right side) of the op-amp as shown.
 - However, **current cannot flow through the switching diode in the direction indicated on the above diagram!** Hence, **no current can flow at all**. Since $I = 0$, $V_n = V_{in}$ by Ohm's law when $I = 0$.
 - But $V_{out} = V_n$. So, finally, $V_{out} = V_{in}$ when $V_{in} > V_{ref}$.
 - In other words, **the low-voltage clipping circuit has no effect on voltages greater than V_{ref}** .
 - Note that for $V_{in} > V_{ref}$, $V_p = V_{ref}$, while $V_n = V_{in}$. Thus, $V_n \neq V_p$ for this case, and the op-amp is *saturated*. (This is because the feedback loop, though present, is interrupted by the switching diode.)
- **If $V_{in} < V_{ref}$**
 - $V_p = V_{ref}$, $V_n = V_p = V_{ref} > V_{in}$, and current tries to flow through resistor R in the direction *opposite* of that indicated on the above diagram.
 - Current tries to flow from the output of the op-amp, through the switching diode, and through the feedback loop.

- In this case, current *can* flow through the switching diode in the direction indicated in the diagram to the right.
- Ideally, there is no voltage drop across the diode; thus, $V_o = V_n$.
- Since the current cannot flow into the inverting input terminal (V_n) of the op-amp, current *must* flow through the resistor in the direction shown here.
- Hence, by Ohm's law, $V_n - IR = V_{in}$. (Since $V_n > V_{in}$, current flows to the left through resistor R as sketched in the circuit diagram to the right.)
- But $V_n \approx V_p = V_{ref}$, and $V_{out} = V_o = V_n$. So, finally, $V_{out} = V_{ref}$ when $V_{in} < V_{ref}$.
- In other words, **the low-voltage clipping circuit clips (to V_{ref}) voltages that are less than V_{ref} .**

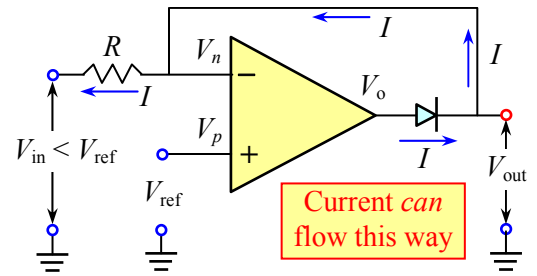


- **Discussion:**

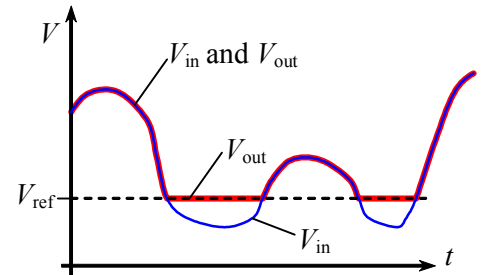- $V_{out} = V_{in}$ as long as V_{in} is greater than V_{ref} . However, if V_{in} drops below V_{ref} , $V_{out} = V_{ref}$. This is what is meant by low-voltage clipping.
- The sketch to the right indicates the clipping.
- Notice that the output follows the input exactly, but every time the input signal drops below V_{ref} , it gets clipped to V_{ref} .




High-voltage clipping circuit

- **Purpose:** To clip voltages above some reference voltage, V_{ref} .
- **Schematic:**
 - The schematic is shown to the right.
 - The high-voltage clipping circuit is identical to the low-voltage clipping circuit, except the switching diode is turned around the opposite way.
- **Analysis:**
 - The analysis is similar, but opposite to that above, and we leave out the details.
 - Results: $V_{out} = V_{ref}$ when $V_{in} > V_{ref}$; current *can* flow through the switching diode in the direction indicated on the schematic. **The high-voltage clipping circuit clips (to V_{ref}) voltages greater than V_{ref} .**
 - $V_{out} = V_{in}$ when $V_{in} < V_{ref}$; current tries to flow the wrong way through the switching diode, but cannot. **The high-voltage clipping circuit has no effect on voltages smaller than V_{ref} .**

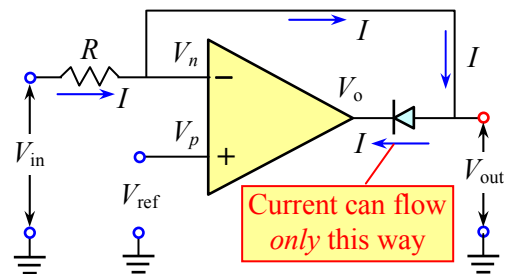

- **Discussion:**

- High-voltage clipping is sometimes necessary to protect electronic components from voltages that are too high.
- For the same input voltage signal as above, the sketch to the right indicates the clipping.
- Every time the input signal rises above V_{ref} , it gets clipped.
- To construct a circuit that clips both high *and* low voltages, we connect a low-voltage clipping circuit and a high-voltage clipping circuit *in series*. In such a case, the reference voltage for the low-voltage clip must be smaller than that for the high-voltage clip.

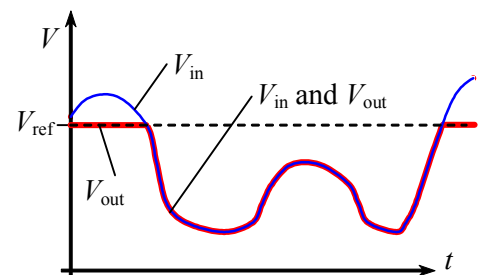


Miscellaneous properties of op-amp circuits

- It is not the intent of this learning module to discuss the internal circuitry of an op-amp.
- However, there are several aspects of actual op-amps that cause problems in circuits – problems that would not exist for ideal op-amps – due to limitations of the internal circuitry of real op-amps. Among these are:
 - Saturation effects (as previously mentioned)
 - Input loading effects (as also previously mentioned)
 - Common-mode rejection ratio (CMRR) effects
 - Gain-bandwidth product (GBP) effects
- The latter two are discussed in detail below.


Common-mode rejection ratio (CMRR)

- **Definition:** *Common-mode rejection ratio* (CMRR) is defined as $\text{CMRR} = 20 \log_{10} \frac{g}{G_{CM}}$, where
 - g is the *open-loop voltage gain* of the op-amp as discussed previously. Another name for g is *differential voltage gain*. In other words, g is the gain in voltage when the input to V_p and V_n are *different*.
 - G_{CM} is the *common-mode voltage gain*. In other words, G_{CM} is the gain in voltage when the input to V_p and V_n are *the same*.
 - The units of CMRR are decibels (dB). A large value of CMRR implies that G_{CM} is small compared to g , which is desirable for rejection of common-mode noise. Modern op-amps have values of CMRR greater than 100 dB.
- **Analysis:**
 - Common-mode gain occurs when the *same* noise (typically high frequency, small amplitude noise) is present in *both* V_p and V_n .
 - For example, consider identical noise at both input terminals of the op-amp, as sketched to the right.
 - Since $V_o = g(V_p - V_n)$, we expect V_o to be exactly zero since $V_p = V_n$ at any instant in time.
 - However, it turns out that the op-amp (due to its internal circuitry – beyond the scope of the present discussion) actually *amplifies* the common-mode noise by factor G_{CM} as sketched.
 - Since noise typically appears in *both* inputs (common-mode input), while the signal typically is wired to only one input (differential-mode input), CMRR needs to be large to ensure a large signal-to-noise ratio at the output of the op-amp.
- **Application:**
 - Which is better – inverting or noninverting op-amp amplifiers?
 - It turns out that there are two competing effects to consider:
 - **Input loading:** Recall that input loading problems occur when the input impedance R_i of an electronic device is not high enough.
 - For a *noninverting op-amp amplifier*, R_i is determined by the internal circuitry of the op-amp, and is generally quite large (of order 1 M Ω).
 - For an *inverting op-amp amplifier*, R_i is largely independent of the internal circuitry of the op-amp, and is instead approximately equal to R_1 (typically of order 10 k Ω to 100 k Ω).
 - Thus, *if input loading is of primary concern, noninverting amplifiers should be used.*
 - **Noise rejection:** As mentioned above, noise generally appears in both input terminals of the op-amp.
 - For a *noninverting op-amp amplifier*, it turns out that in many applications, the noise amplitude is *nearly the same* in the V_p and V_n input terminals, and thus *common-mode gain is more of a problem in these circuits.*
 - For an *inverting op-amp amplifier*, it turns out that the noise amplitude is generally greater in the V_n input terminal than in the V_p input terminal (since the V_p input terminal is grounded), and thus *common-mode gain is less of a problem in these circuits.*
 - Thus, *if noise reduction and signal-to-noise issues are of primary concern, inverting amplifiers should be used.*

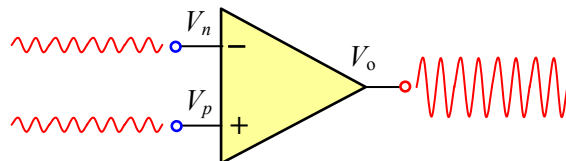

Gain-bandwidth product (GBP)

- **Definition:** *Gain-bandwidth product* (GBP), also called simply *bandwidth* is defined as $\text{GBP} = G_{\text{theory}} \cdot f_c$, where
 - G_{theory} is the *theoretical gain* of the op-amp amplifier as discussed previously, and given the symbol G .
 - f_c is the *internal cutoff frequency* of the op-amp itself.
 - For a given op-amp, GBP is a constant – it is one of the specifications supplied by the op-amp manufacturer. The GBP of modern op-amps is typically on the order of 1.0 MHz, and is often listed as simply *bandwidth*.
 - The units of GBP are the same as those of frequency.
 - Without going into details, *the inner circuitry of an op-amp acts like a first-order low-pass filter (with cutoff frequency f_c) when very high frequency inputs are applied.*

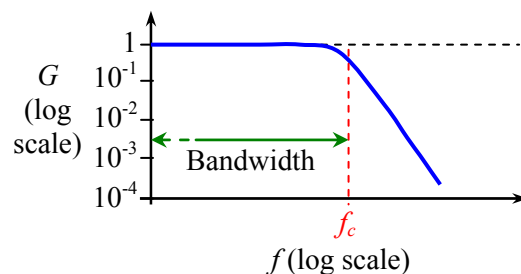

- So, the actual gain of the op-amp amplifier drops off at high frequencies, just like a low-pass filter, as sketched above for the case in which G_{theory} is 1.
- The range of frequencies from 0 Hz (DC) to internal cutoff frequency f_c is called the **bandwidth**. In some electronics literature, the bandwidth is defined simply as f_c itself, **bandwidth = f_c** when $G_{\text{theory}} = 1$.
- Equations for the internal low-pass filtering effects of the op-amp are the *same* as those for first-order low-pass Butterworth filters except that f_c rather than f_{cutoff} is the cutoff frequency. E.g., the gain G_{GBP} due to internal low-pass filtering effects is $G_{\text{GBP}} = \frac{1}{\sqrt{1+(f/f_c)^2}}$, where f is the input signal frequency.
- GBP effects are related to the op-amp's **slew rate**, defined as *the rate of change in output voltage when the input is a step change of voltage*. The units of slew rate are typically volts per microsecond (V/ μ s).

- **Analysis:**

- We now compare GBP effects for inverting and noninverting op-amp amplifiers.

- **Noninverting op-amp amplifier:**

- The theoretical gain (no GBP effects) of a noninverting op-amp amplifier is $G_{\text{theory}} = 1 + \frac{R_2}{R_1}$.
- We define $\text{GBP}_{\text{noninverting}}$ as the **noninverting gain-bandwidth product** of the op-amp. *Note: This is the same as the GBP value supplied by the op-amp manufacturer in their list of specifications.*
- The equation for GBP is written as $\text{GBP}_{\text{noninverting}} = G_{\text{theory}} \cdot f_c$, from which the internal cutoff frequency can be calculated (for known values of $\text{GBP}_{\text{noninverting}}$ and G_{theory}).
- The *actual* gain of a noninverting op-amp amplifier is thus *less* than the theoretical gain, namely,

$$G = G_{\text{theory}} G_{\text{GBP, noninverting}} = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{\sqrt{1+(f/f_c)^2}} \quad \text{where} \quad f_c = \frac{\text{GBP}_{\text{noninverting}}}{G_{\text{theory}}}$$

- Consider for example a 741 op-amp with $\text{GBP}_{\text{noninverting}} = \text{GBP}_{\text{manufacturer spec}} = 1.0 \text{ MHz}$. For a theoretical gain of 10, the internal cutoff frequency of the op-amp is thus $f_c = \text{GBP}_{\text{noninverting}}/G_{\text{theory}} = (1.0 \text{ MHz})/10 = 0.10 \text{ MHz} = 100,000 \text{ Hz}$. But **f_c is not a constant – it depends on G_{theory}** .
- As we increase the theoretical gain, f_c must decrease. For this example op-amp, when $G_{\text{theory}} = 100$, $f_c = 10,000 \text{ Hz}$, and when $G_{\text{theory}} = 1000$, $f_c = 1,000 \text{ Hz}$. In other words, **the larger the theoretical gain of the amplifier, the lower the internal cutoff frequency (bandwidth) of the amplifier.**

- **Inverting op-amp amplifier:**

- The theoretical gain (no GBP effects) of an inverting op-amp amplifier is $G_{\text{theory}} = -\frac{R_2}{R_1}$.
- We define $\text{GBP}_{\text{inverting}}$ as the **inverting gain-bandwidth product** of the op-amp (a negative quantity), $\text{GBP}_{\text{inverting}} = -\frac{R_2}{R_1 + R_2} \text{GBP}_{\text{noninverting}}$. *Note: This is not the same as the GBP value supplied by the op-amp manufacturer in their list of specifications.*
- The equation for GBP is written as $\text{GBP}_{\text{inverting}} = G_{\text{theory}} \cdot f_c$, from which the internal cutoff frequency is determined (for known values of $\text{GBP}_{\text{inverting}}$ and G_{theory}).
- The *actual* gain of an inverting op-amp amplifier is thus *less* than the theoretical gain, namely,

$$G = G_{\text{theory}} G_{\text{GBP, inverting}} = -\frac{R_2}{R_1} \frac{1}{\sqrt{1+(f/f_c)^2}} \quad \text{where} \quad f_c = \frac{\text{GBP}_{\text{inverting}}}{G_{\text{theory}}}$$

- As with a noninverting op-amp amplifier, when we increase the theoretical gain of an inverting op-amp amplifier, f_c must decrease. Again, as above, **the larger the theoretical gain of the amplifier, the lower the internal cutoff frequency (bandwidth) of the amplifier.**
- For either case (inverting or noninverting amplifier), we see, therefore, that **it is futile to try to amplify a very high frequency signal by a very large gain using only one op-amp** – the internal low-pass filtering effects quickly overpower the theoretical gain of the amplifier.
- Solution? **Use two (or more) op-amp amplifiers in series.** Some examples will be shown in class.